



EX2: serie oscillateur Libre

1)  $Y_A \rightarrow u(t) = u_{R1}(t) + u_{R2}(t)$

$Y_B \rightarrow u_{R1}(t) =$

à t=0  $\Rightarrow i=0 \Rightarrow u_{R2}(0) = 0 \Rightarrow$

$\mathcal{L}_1 \rightarrow u_{R1}(t)$

$\mathcal{L}_2 \rightarrow u_{R2}(t) = u(t)$

2) loi de Maille :

$u_{R1} + u_{R2} + u_L = E$

$(R_1 + R_2 + r)i + L \frac{di}{dt} = E$

En Régime Permanent :

$i = \text{cte} \Rightarrow \frac{di}{dt} = 0$

$\Rightarrow I_p = I_0 = \frac{E}{R_1 + R_2 + r}$

3) loi de Maille :

on pose  $R_T = R_1 + R_2 + r$

$(R_T i + L \frac{di}{dt} = E) \times R_1$

$R_T u_{R1} + L \frac{du_{R1}}{dt} = R_1 E$

$u_{R1} = E - u$

$R_T(E - u) + L \frac{d(E - u)}{dt} = R_1 E$

$R_T E - R_T u - L \frac{du}{dt} = R_1 E$

$R_T u + L \frac{du}{dt} = E(R_T - R_1)$

$R_T u + L \frac{du}{dt} = (R_2 + r) \times E$

$u + \frac{L}{R_T} \frac{du}{dt} = \frac{R_2 + r}{R_T} E$

équation différentielle

b)  $u(t) = A + B e^{-t/\tau}$  est sol<sup>o</sup>

avec  $\tau = \frac{L}{R_T}$

Remplaçant dans

à t=0 :  $u(0) = u_{R1}(0) + u_{R2}(0) = E$

$A + B = E \Rightarrow A = E - B$

Remplaçant dans l'éq. diff :

$E - B + B e^{-t/\tau} + \tau \times (-1/\tau) B e^{-t/\tau} = \frac{R_2 + r}{R_T} E$

$\Rightarrow B = E - \frac{R_2 + r}{R_T} E = \frac{R_1}{R_T} E = R_1 I_0$

$A = E - B = E - \frac{R_1}{R_T} E = \frac{R_2 + r}{R_T} E = (R_2 + r) I_0$

$\Rightarrow u(t) = (R_2 + r) I_0 + R_1 I_0 e^{-t/\tau}$

c)  $u_{R1} = E - u$

$u_{R1} = E - \frac{R_2 + r}{R_T} E - \frac{R_1}{R_T} E e^{-t/\tau}$

$u_{R1}(t) = \frac{R_1}{R_T} E - \frac{R_1}{R_T} E e^{-t/\tau}$

$u_{R1}(t) = \frac{R_1}{R_T} E (1 - e^{-t/\tau})$

$u_{R2}(t) = R_1 I_0 (1 - e^{-t/\tau})$

4)  $U_{Bp} = 0,2V$  et  $I_0 = I_p = 40mA$

$U_{Bp} = r I_0 \Rightarrow r = \frac{U_{Bp}}{I_0} = \frac{0,2}{40 \cdot 10^{-3}}$

$r = 5 \Omega$

o D'après la courbe  $\mathcal{L}_2 \Rightarrow U_p = 2V$

$\Rightarrow U_{R2p} = U_p - U_{Bp} = 2 - 0,2 = 1,8V$

$\Rightarrow R_2 I_p = 1,8 \Rightarrow R_2 = \frac{1,8}{40 \cdot 10^{-3}}$

$R_2 = 45 \Omega$





5) à  $t = t_1 \Rightarrow u(t) = u_{R_1}(t)$

a)  $u + u_{R_1} = E \Rightarrow 2u_{R_1} = E$

$u_{R_1}(t_1) = \frac{E}{2} \Rightarrow$

$\frac{R_1 E}{R_T} (1 - e^{-t_1/\tau}) = \frac{E}{2}$

$1 - e^{-t_1/\tau} = \frac{R_T}{2R_1}$

$e^{-t_1/\tau} = 1 - \frac{R_T}{2R_1} = \dots$

$= \frac{2R_1 - R_1 - R_2 - r}{2R_1}$

$= \frac{R_1 - R_2 - r}{2R_1}$

$-\frac{t_1}{\tau} = \ln\left(\frac{R_1 - R_2 - r}{2R_1}\right)$

$t_1 = -\tau \ln\left(\frac{R_1 - R_2 - r}{2R_1}\right)$

$u_{R_1}(t_1) = \frac{R_1 E}{R_T} \left(1 - e^{\ln\left(\frac{R_1 - R_2 - r}{2R_1}\right)}\right)$

$u_{R_1}(t_1) = \frac{R_1 E}{R_T} \left[1 - \frac{R_1 - R_2 - r}{2R_1}\right]$

$= \frac{R_1 E}{R_T} \left[\frac{2R_1 - R_1 + R_2 + r}{2R_1}\right]$

$= \frac{R_1 E}{R_T} \times \frac{R_T}{2R_1} = \frac{E}{2}$

$\Rightarrow E = 2u_{R_1}(t_1) = 2 \times 3 = 6V$

c)  $u_{R_1,p} = E - u_p = 6 - 2 = 4V$

$R_1 I_0 = u_{R_1,p} \Rightarrow R_1 = \frac{u_{R_1,p}}{I_0}$

$R_1 = \frac{4}{40 \cdot 10^{-3}} = 100 \Omega$

$\tau$  est l'abscisse du pt d'intersection de la tangente à l'origine

à la Courbe  $u_{R_1}(t)$  avec la dro. G  $u_{R_1,p} = 4V \Rightarrow$

$\tau = 2ms = 2 \cdot 10^{-3}s$


$L = \tau \times R_T = 2 \cdot 10^{-3} (100 + 40 + 10)$

$L = 0,3H$

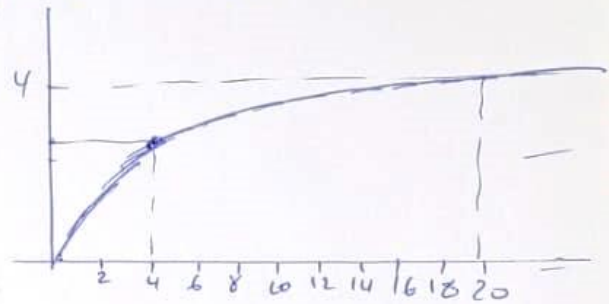6)  $L' = 2L \Rightarrow \tau' = 2\tau = 4ms$

$\Rightarrow 5\tau' = 5 \times 4 = 20ms$

pour  $t = \tau' \Rightarrow u_{R_1}(\tau') = 0,63 \times 4 = 2,5V$



B) 1) loi de Maillet:

$(R_2 + r) i + u_C + L \frac{di}{dt} = 0$

$u_C + (R_2 + r) C \frac{du_C}{dt} + LC \frac{d^2 u_C}{dt^2} = 0$

2) Libre ———  
Amorti ———

3) a)  $E_T = E_C + E_L = \frac{1}{2} C u_C^2 + \frac{1}{2} L i^2$

$\frac{dE_T}{dt} = -(R_2 + r) i^2 < 0 \Rightarrow E_T \searrow$

4)  $T_0^2 = 4\pi^2 LC \Rightarrow C = \frac{T_0^2}{4\pi^2 L}$

$C = \frac{(8 \cdot 10^{-3})^2}{4\pi^2 \times 0,3} = 5,4 \times 10^{-6} F$

5)  $W_d = E_T(0) - E_T(t_1)$

$\bullet E_T(0) = \frac{1}{2} C U^2 = \frac{1}{2} \times 5,4 \times 10^{-6} \times 12^2 = 3,88 \cdot 10^{-4} J$

$\bullet E_T(t_1) = \frac{1}{2} C u_C^2(t_1) + \frac{1}{2} L i^2$

$i(t_1) = C \frac{du_C}{dt}(t_1) = C \exp(-t/\tau)$

